

ECE 490-ST

Wireless Computing

Lesson 6 :: Impedance Transforming

Eyeballing impedance shifts

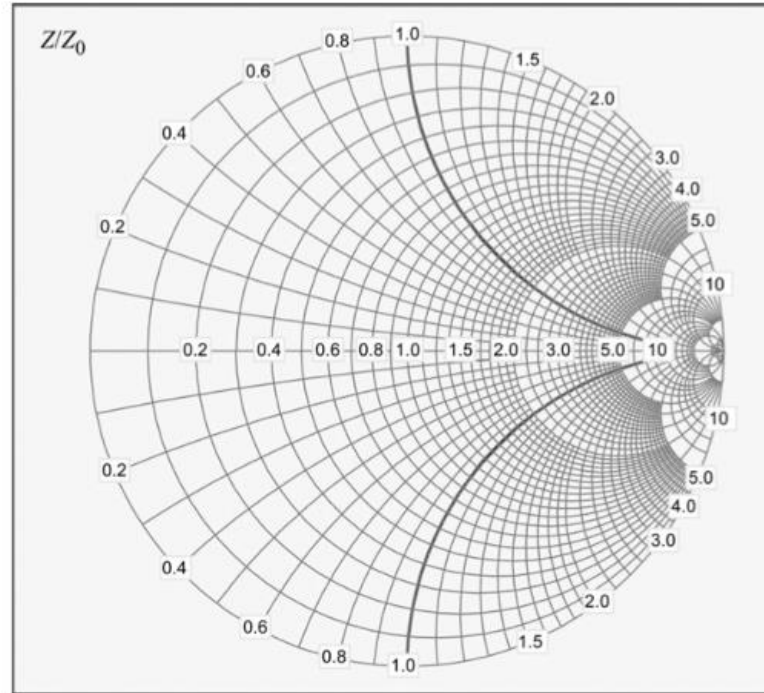


Figure A4.4



Valparaiso
University

Eyeballing Impedance Shifts

- If Gamma moves .25 around the Smith chart —

- $X = j \omega L$

- $X = -j / (\omega C)$

- $X = \omega L$

- $X = -1 / (\omega C)$

- $L = (X * Z_0) / \omega$

- $C = -1 / (Z_0 * X * \omega)$

$$L = \frac{0.25 * 50}{2\pi(915e6)} \\ = 1.4 \text{ nH}$$

- EX: We move from 0 -> 1.1. At 915 MHz:

- $L = (1.1 * 50) / (2 * \pi * 915e6)$


- $L = 9.566 \text{ nH}$

VNA DEMO

What is my hand acting like?


What is the value of my hand?

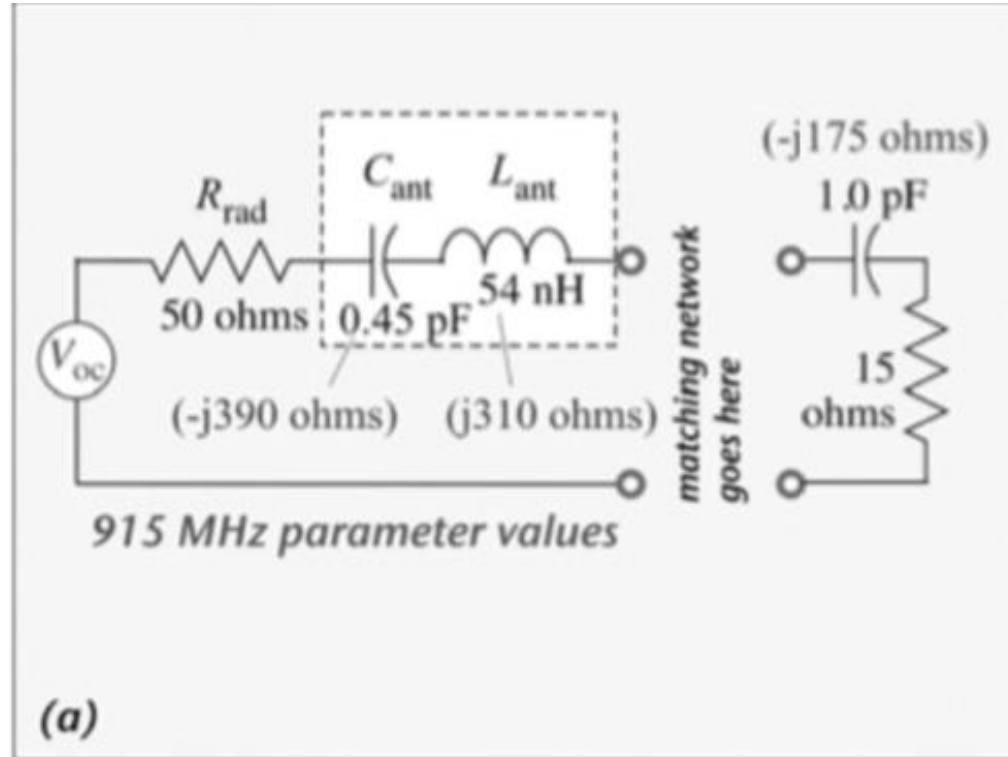I want the load to appear as the conjugate of source




IMPEDANCE TRANSFORMING

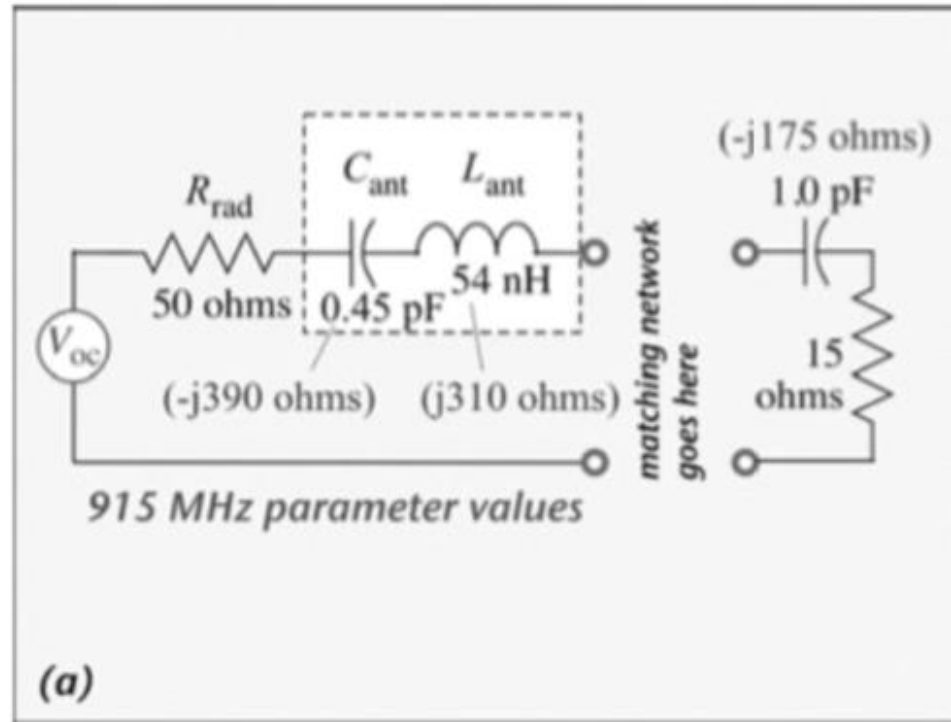- What is Gamma when looking into the source?
- What is the conjugate of the input Gamma?
- What is Gamma when looking into the load?
- Which way do we need to rotate?
- Can we get there with 1 element?
- What other element do we need?



Transforming impedances

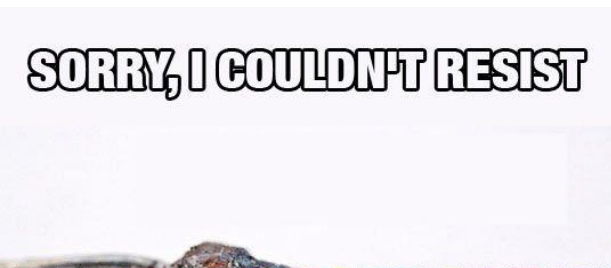- For impedance transformation networks, **we will only use L and C**
- These elements do not absorb energy.
- However, the job of a RESISTOR is to convert current into heat.
- We do not want that
- We don't want to lose power.
- So, **NO RESISTORS** in impedance transformation circuits




For homework¹



- Be ready to find networks (circuits) that can transform impedances.
- By inspection and small calculations
- Verify with numerical tool (MATLAB) and plotting tools (Your handy dandy Smith chart)

¹ At least a part of it

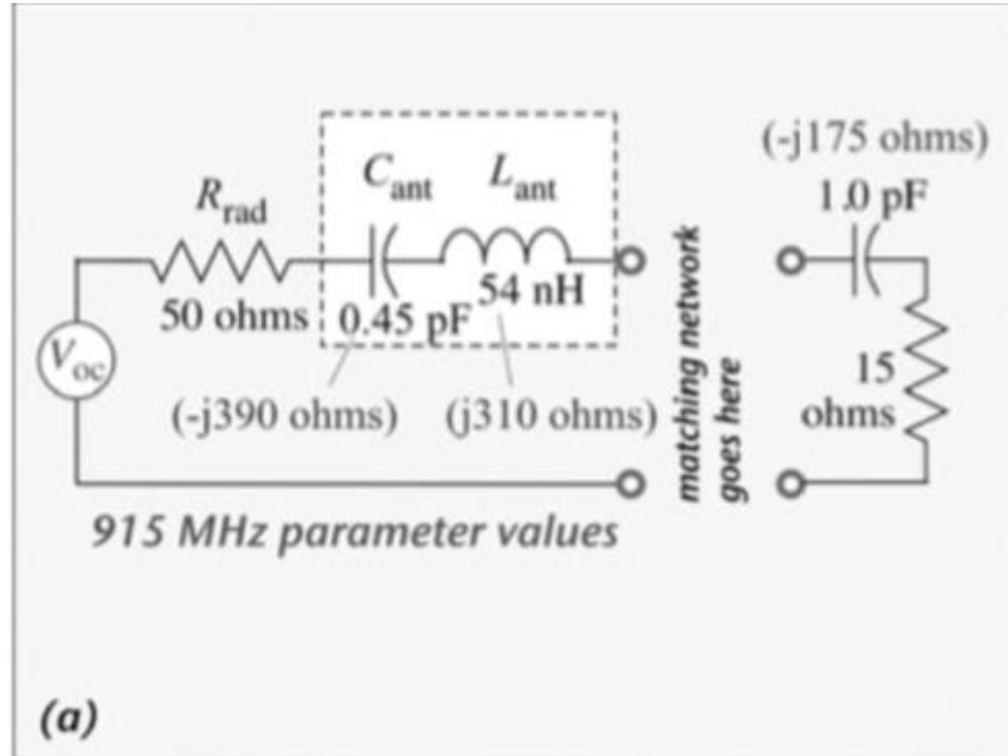I want the load to appear as the conjugate of source



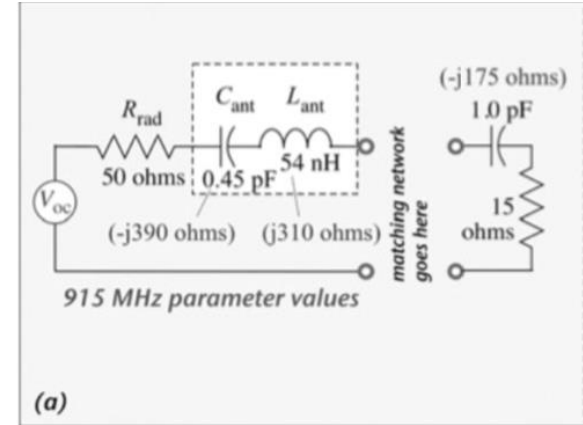
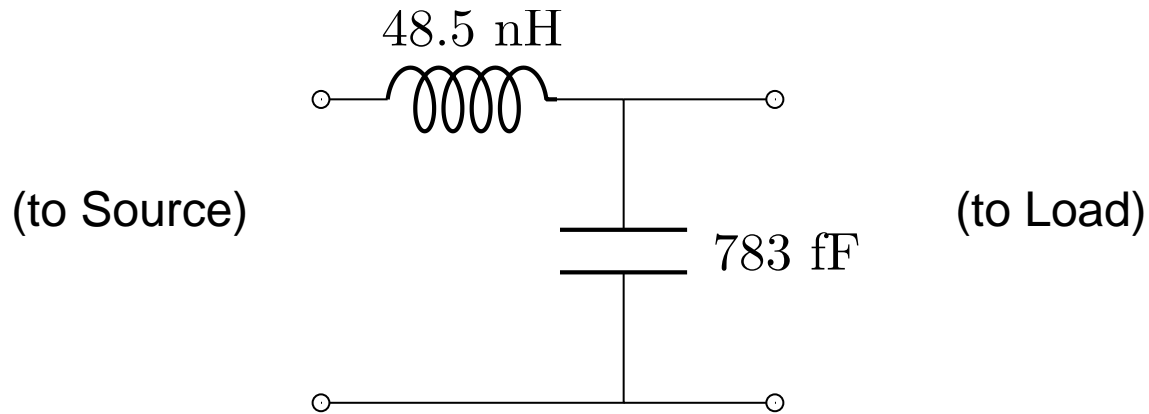
I want the load to appear as the conjugate of source





I want

(to Source)



source

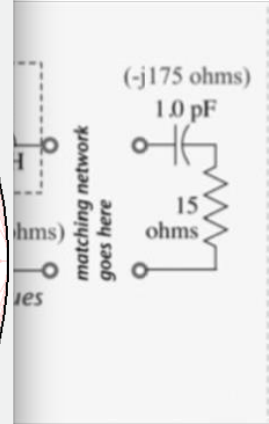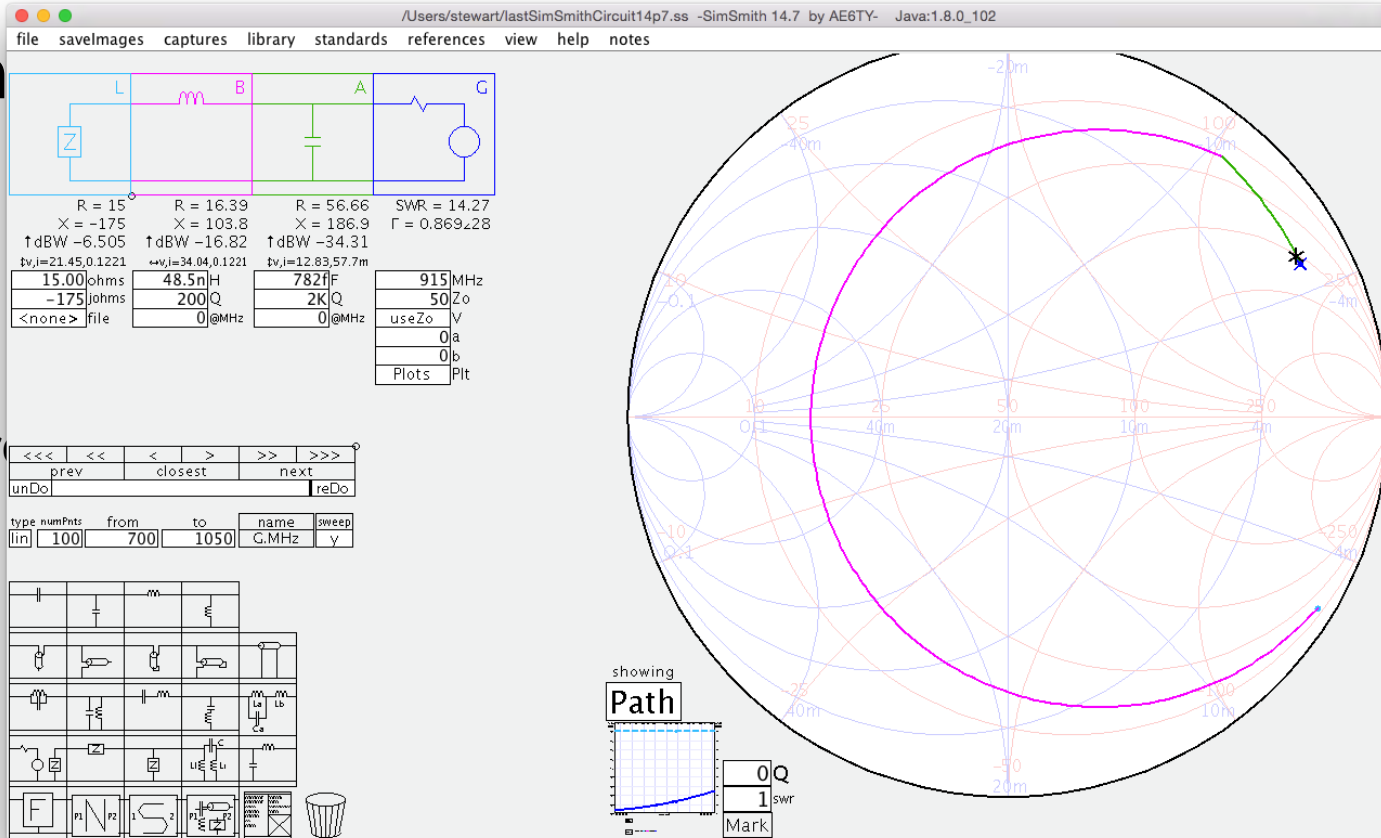

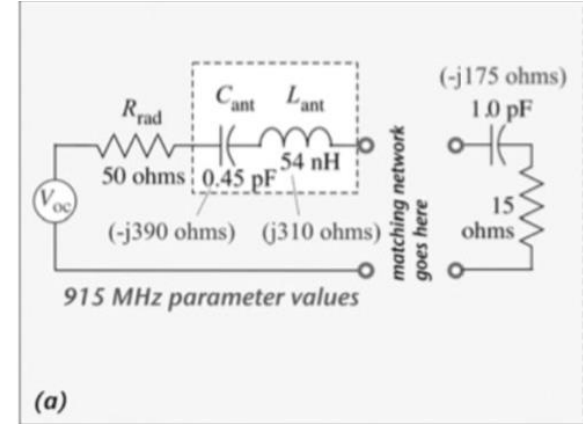
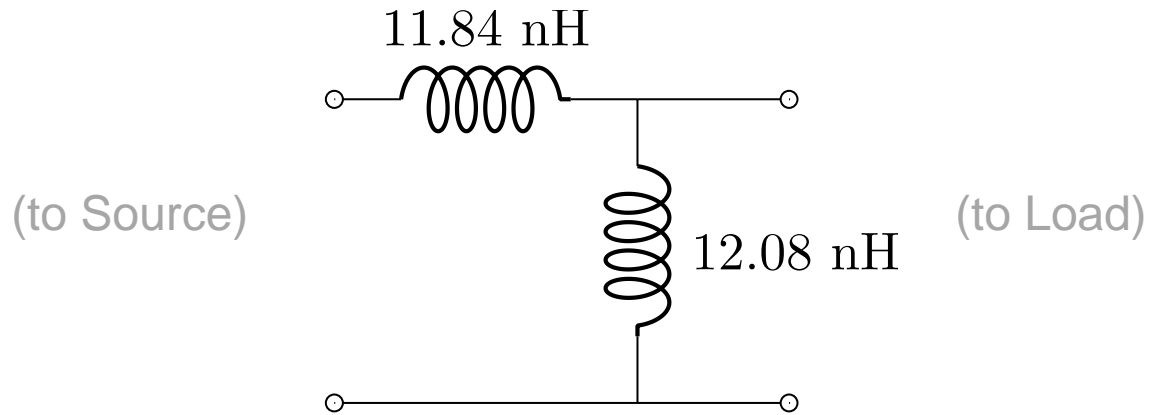
I want the load to appear as the conjugate of source



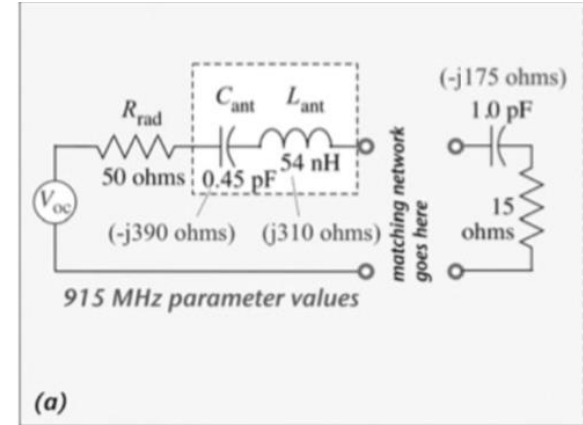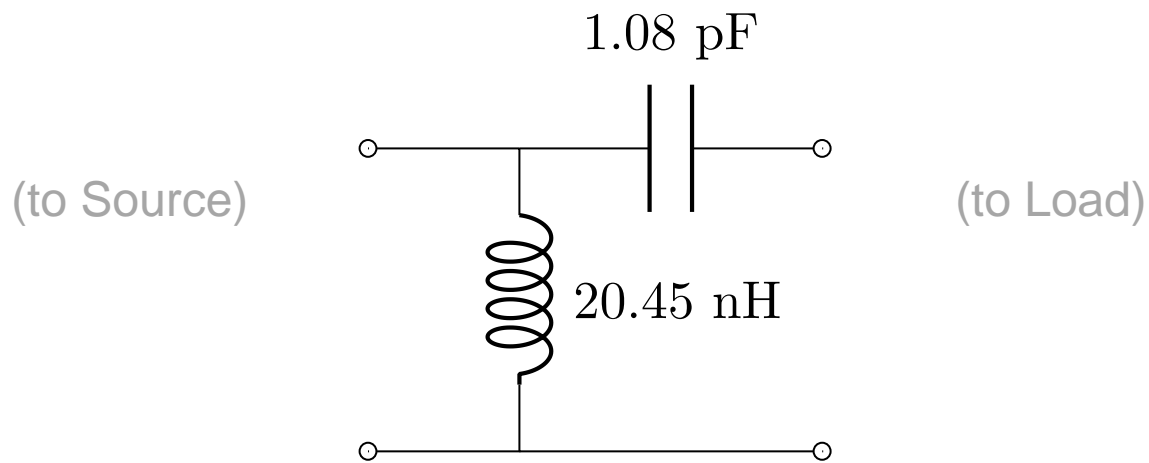I want the load to appear as the conjugate of source




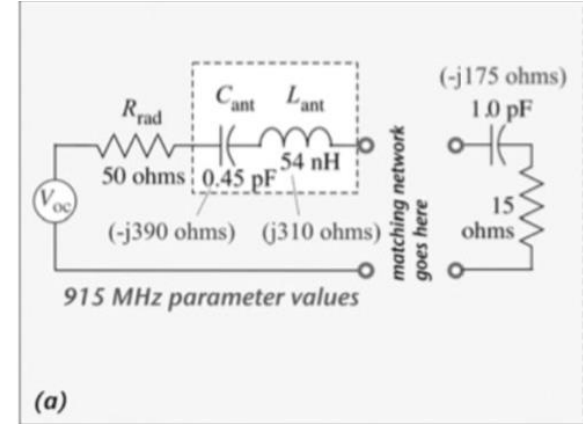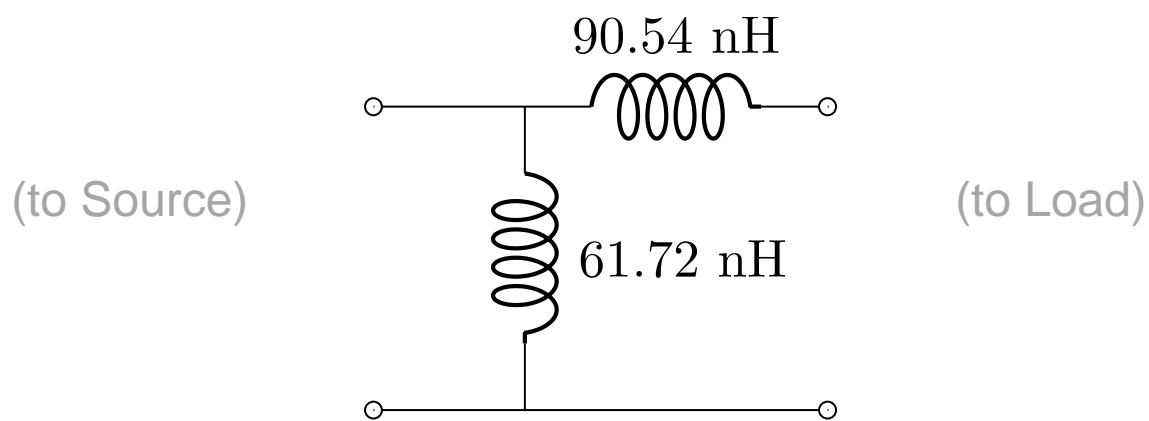I want the load to appear as the conjugate of source




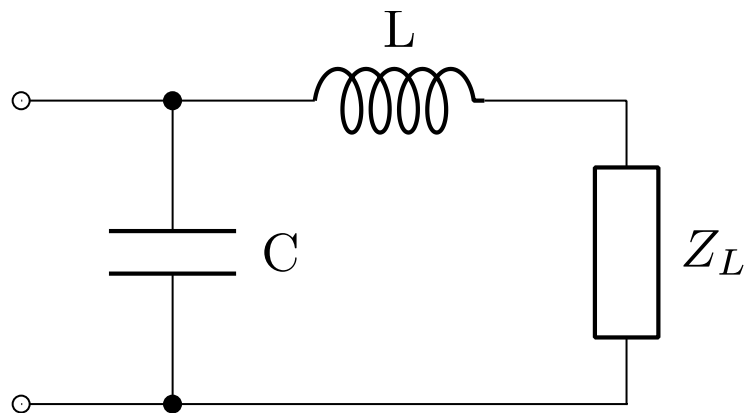Example

Two networks are shown below. 1) Select the one that can transform $Z_L = 38.5 + j57.7$ to 50 Ohm. 2) Find the element values at $f = 1 \text{ GHz}$



A

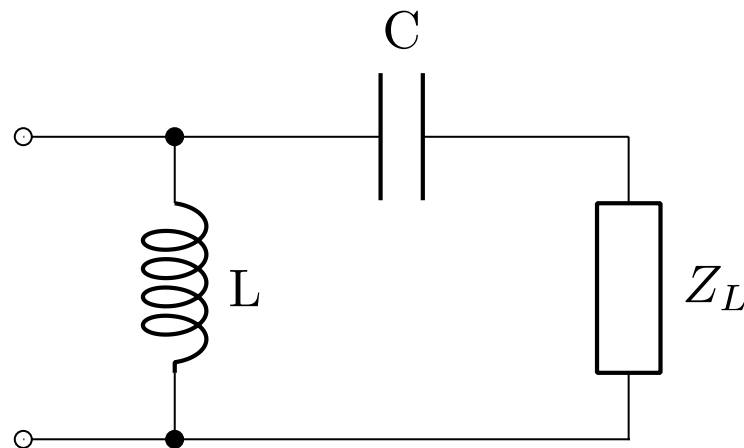

B

Introducing Q

- ¿Qué?



Introducing Q

- Not him either




Introducing Q – the Quality Factor

- Q let's us quantify the bandwidth of a network



Introducing Q – the Quality Factor

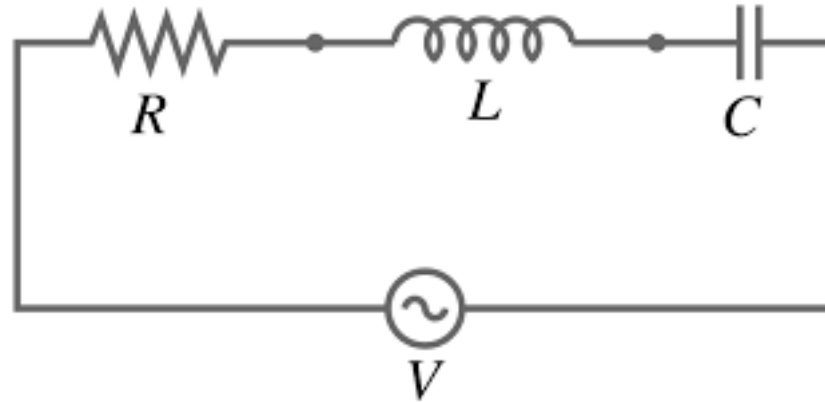- Q let's us quantify the bandwidth of a network




- Take an RLC circuit

$$Z = R + j\omega L - \frac{j}{\omega C}$$

Introducing Q – the Quality Factor

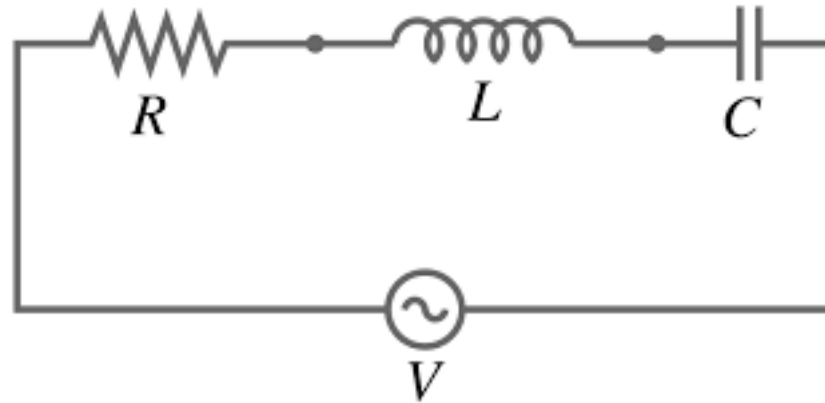- Q let's us quantify the bandwidth of a network




$$W_{res} L = \frac{1}{W_{res} C}$$

$$W_{res} = \sqrt{\frac{1}{LC}}$$

$$Z = R + j\omega L - \frac{j}{\omega C}$$

Introducing Q – the Quality Factor

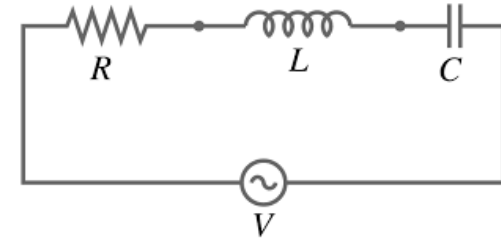- Q let's us quantify the bandwidth of a network
- The ratio of reactance to resistance is Q.
- The lower the resistance, the less energy loss
- Q is inversely proportional to Bandwidth
- High Q means a narrower bandwidth
- For you, it just means you can calculate resistance



$$Z = R + j\omega L - \frac{j}{\omega C}$$

$$\omega_{res} L = \frac{1}{\omega_{res} C}$$

$$Q = \frac{\omega_{res} L}{R} \quad \text{or} \quad \omega_{res} = \sqrt{\frac{1}{LC}}$$

$$= \frac{1}{\omega_{res} C R}$$

Introducing Q – the Quality Factor

- For you, it just means you can calculate resistance

$$Q = \frac{\omega_{\text{res}} L}{R}$$
$$= \frac{1}{\omega_{\text{res}} C R}$$

$$\omega_{\text{res}} L = \frac{1}{\omega_{\text{res}} C}$$
$$\Rightarrow \omega_{\text{res}} = \sqrt{\frac{1}{LC}}$$

Introducing Q – the Quality Factor

- For you, it just means you can calculate resistance

$$Q = \frac{\omega_{\text{res}} L}{R}$$
$$= \frac{1}{\omega_{\text{res}} C R}$$

- For a capacitor: $R = \frac{1}{2\pi f C Q}$


- Find R, then add back into circuit in series with the capacitor

$$\omega_{\text{res}} L = \frac{1}{\omega_{\text{res}} C}$$
$$\Rightarrow \omega_{\text{res}} = \sqrt{\frac{1}{LC}}$$


Designing Transformation Networks

- Most inductors or capacitors will specify a Q value.
- You do not have access to *every possible* L and C value
- Need to get as close as possible.
- Common Networks are


TEE Network

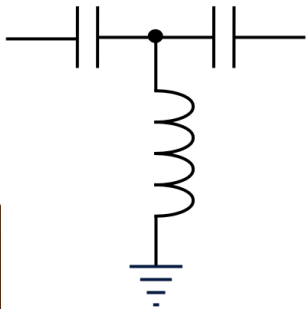

PI Network

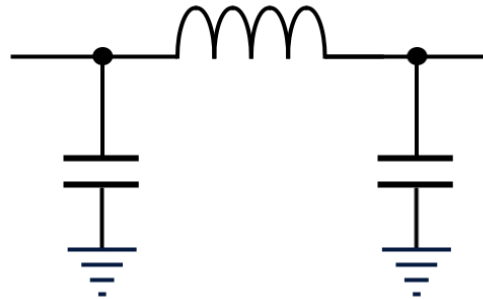

L Network

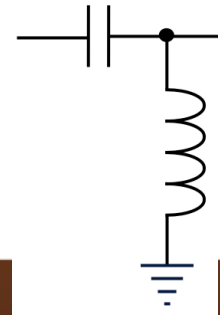

Valparaiso
University

Useful equations to know

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Given load
impedance,
Find reflection
coefficient

$$Z_L = Z_0 \frac{1 + \Gamma}{1 - \Gamma}$$

Given reflection
coefficient,
Find load
impedance

$$Q = \frac{\omega L}{R} \\ = \frac{1}{\omega C R}$$

Given Q &
frequency, solve
to find series R

For Homework (the 2nd part)

- Design a network to transform the load impedance to 50 Ohms (at 915 MHz)
 - You are limited to L and C only, and only a small set of values
 - Find the network that you think works best and justify this (i.e., compare to other networks)
 - Once you've designed your network, implement the network and use MATLAB to apply it to the measured data to predict how it will perform.

Useful links

- **Online impedance matching designer**
- <https://home.sandiego.edu/~ekim/e194rfs01/jwmatcher/matcher2.html>
- NOTE: This designer transforms to the *CONGUGATE* of the source. So to match to " $Z_{new} = 80 + j90$ " you would enter source resistance as "80" and source reactance as "-90".
- **SimSmith downloadable tool**
- http://www.ae6ty.com/smith_charts.html
- Direct link for Windows x64 [mac and linux versions also available]
- http://www.ae6ty.com/Smith_Charts_files/SimSmith_windows-x64_14_7.exe