

ECE 490-ST

Wireless Computing

Lesson 10a :: Matching boards

Step 1

Measure the boards

Step 1

Measure the boards


Step 0

Calibrate the VNA

Removes unintended errors

Gives “true” impedance measurement

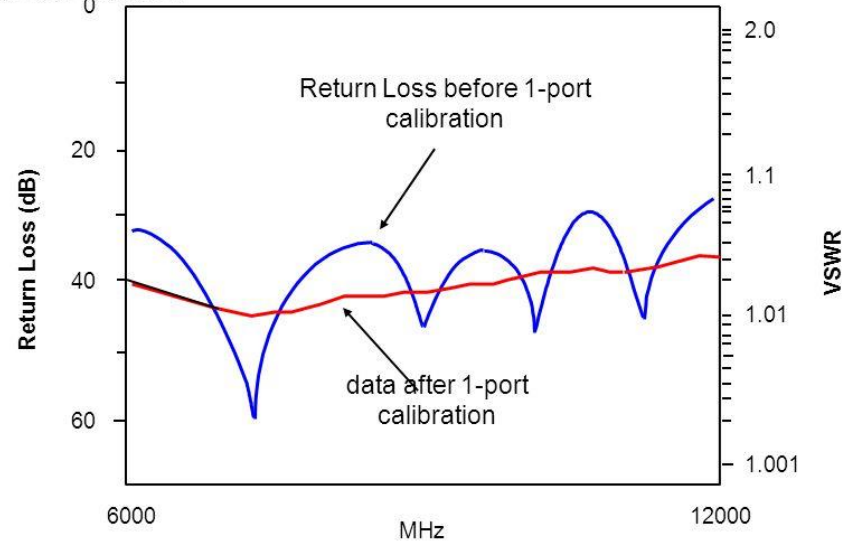Return Loss (Match) Before and After One-Port Calibration



Step 0


Calibrate the VNA

Removes unintended errors

Gives “true” impedance measurement

Calibrate with 3 known impedances

Typically, Open, Short, Load

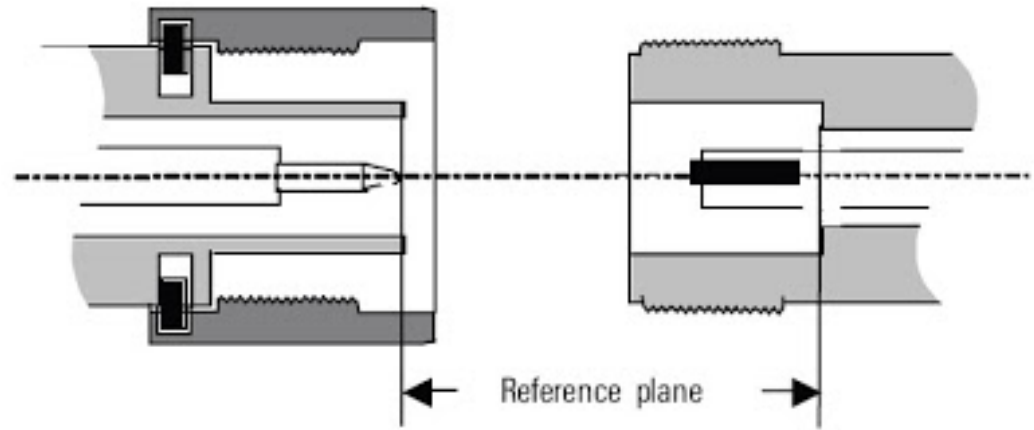

*Location of the reference plane
in a Type-N connector*




Valparaiso
University

Step 1

Measure the boards

$$Z_L = 1.6 - j39.6$$

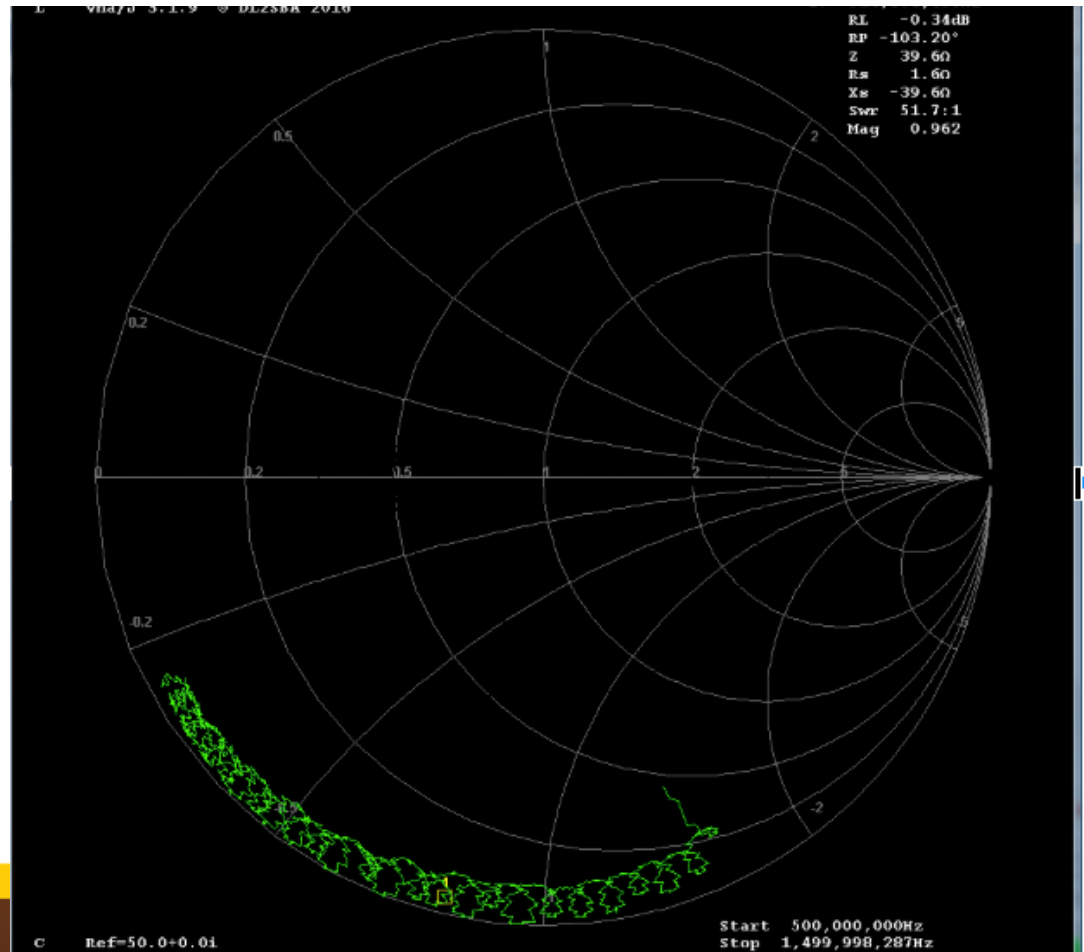

Valparaiso
University


Step 3

Design a matching network

Goal of matching to 50Ω

Series L, Shunt C

Use 10 nH first

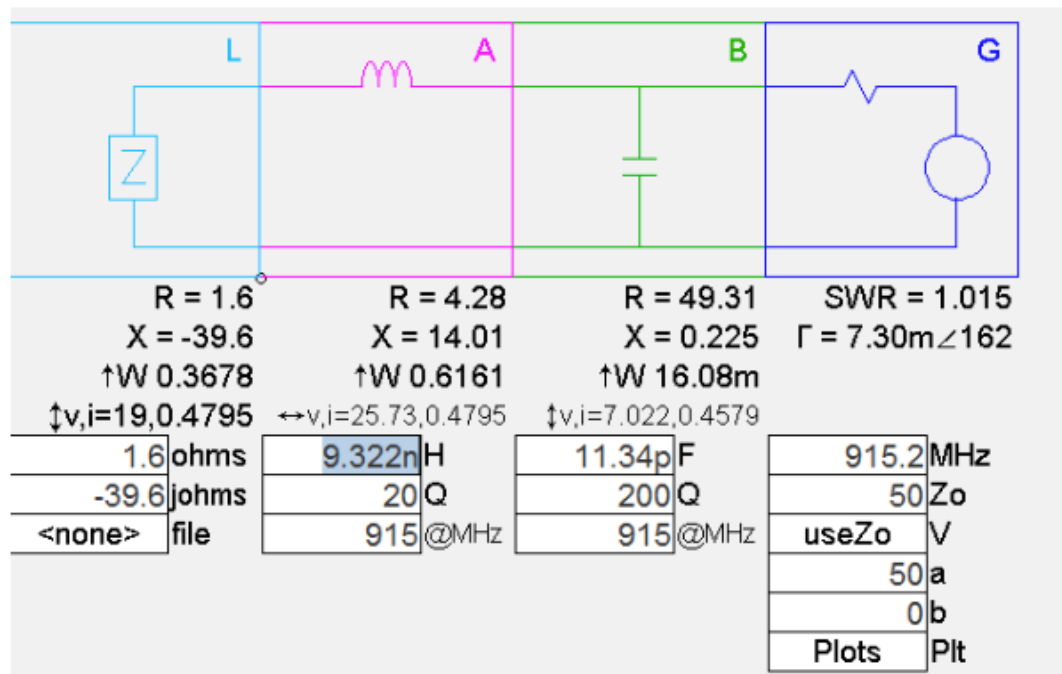

Step 4


Start implementing!

L moves to $2.9 + j19.5$

Wanted: $4.2 + j14$

L appears as 10.4 nH w/ $Q=43$

Try 8.2 nH!

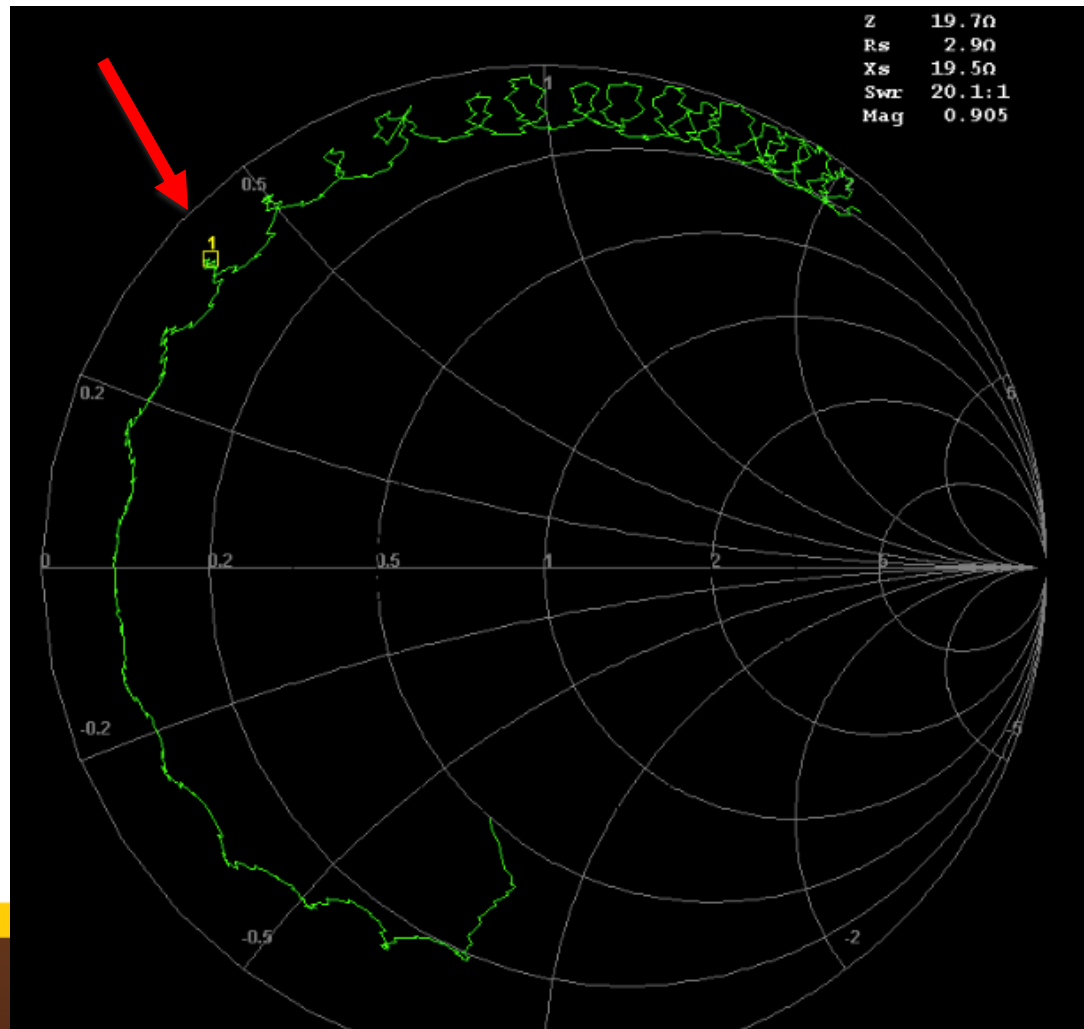


Step 4

Start Implementing!

End up at $3.3 + j5.2$ – Too low!

Appears as L of 8.02 nH with Q of 24.4

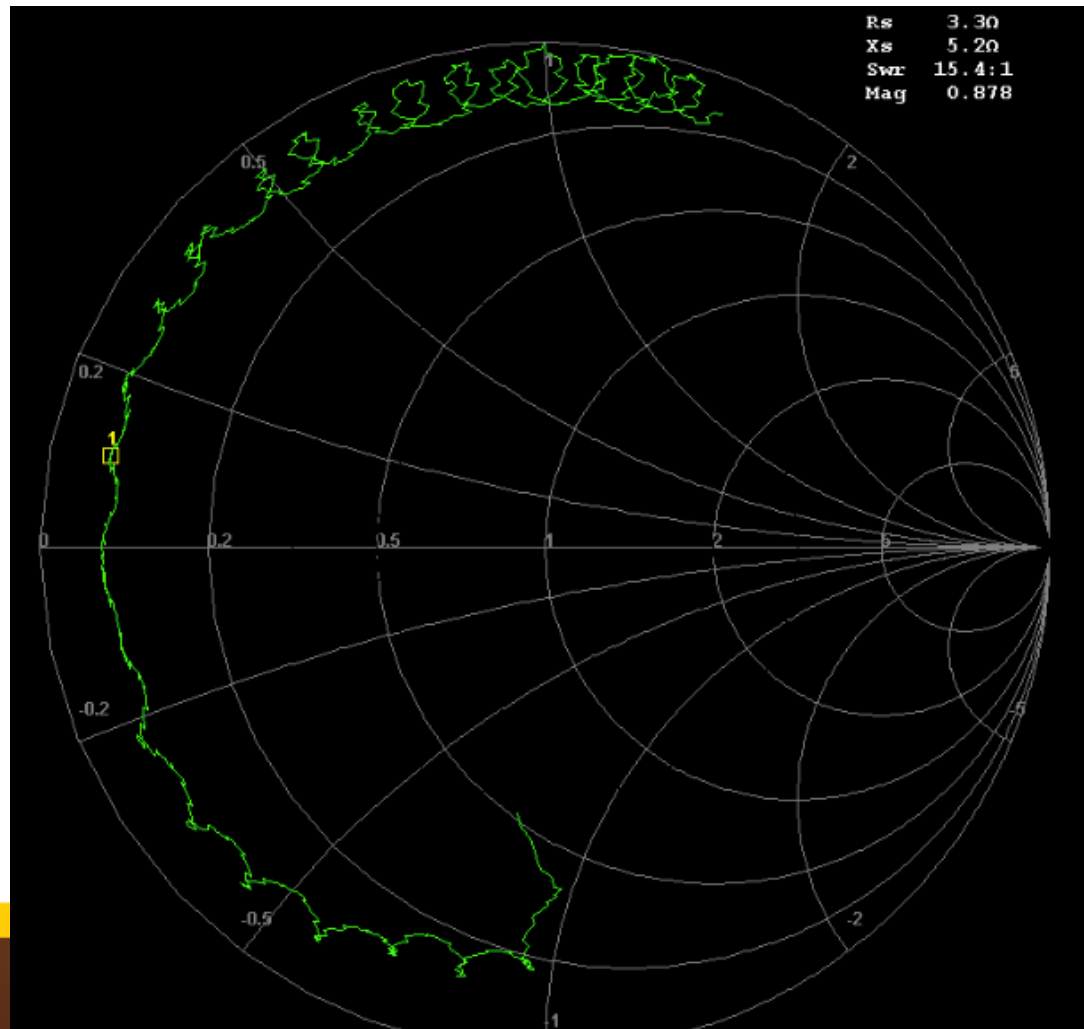


Step 3 (again)

Design a matching network.

Add in a shunt 0.8 pF C next to the load (to counteract parasitics)

Now at, $2.3 + j11.5$


Looks good!

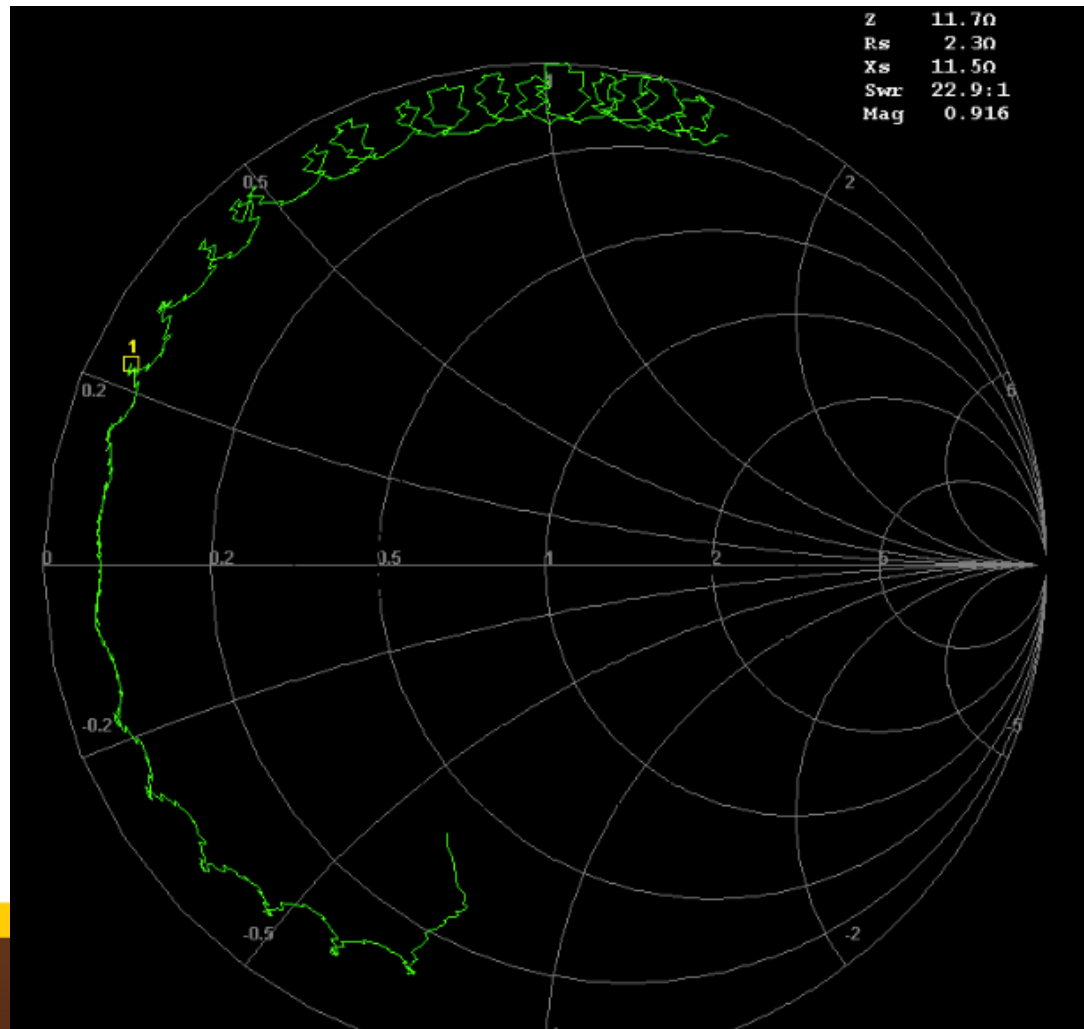

Step 3 (again)

Update your matching network

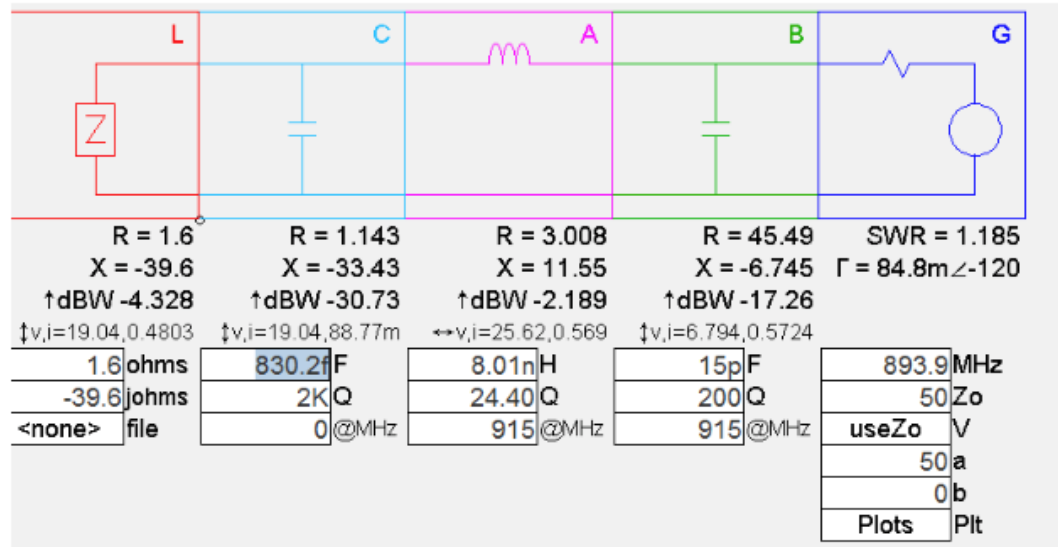(includes any “fudge factors” that you’ve found already)




Step 4 Implement it!

Keep implementing changes, reading values from VNA, and moving forward.

(Or rather, backward to the generator)

Add in the last change, and

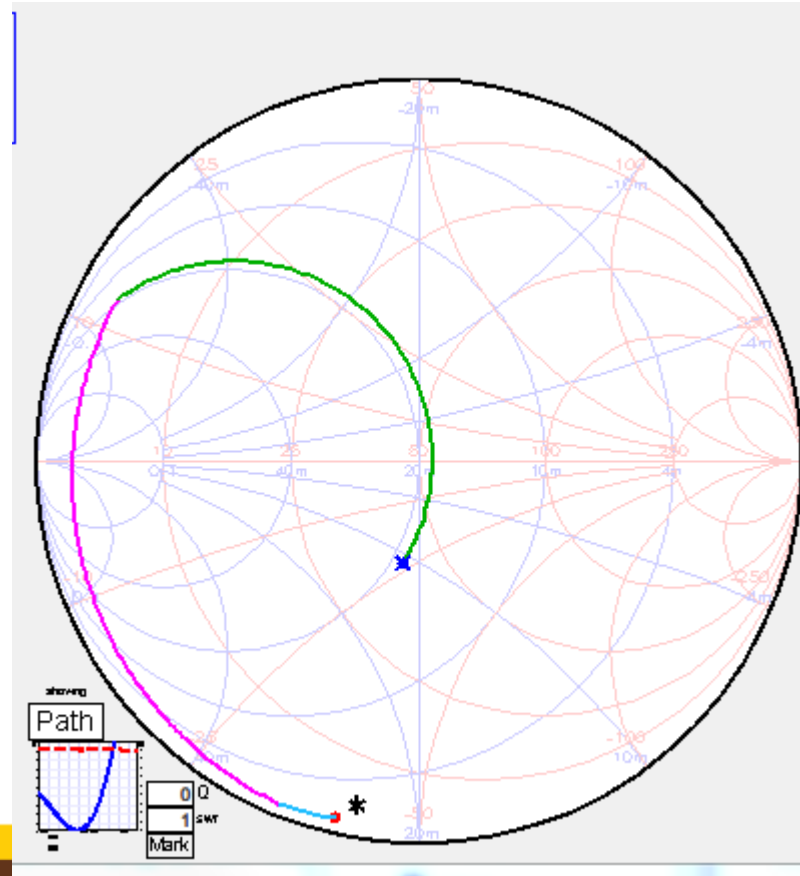


Step 4 Implement it!

Keep implementing changes,
reading values from VNA, and
moving forward.

(Or rather, backward to the
generator)

Add in the last change, and


WAT?

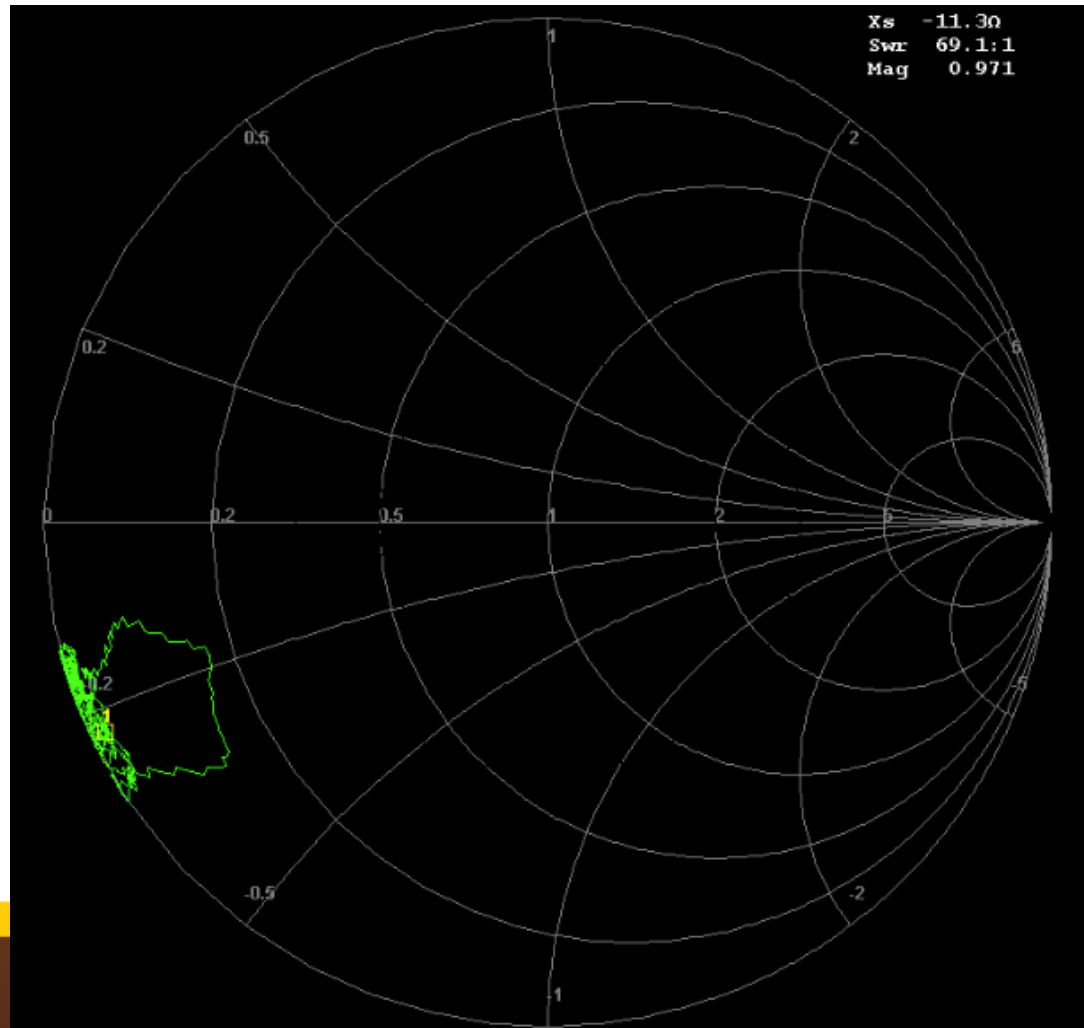

Go back to step 1

Start with a new network.
Forget this old one.

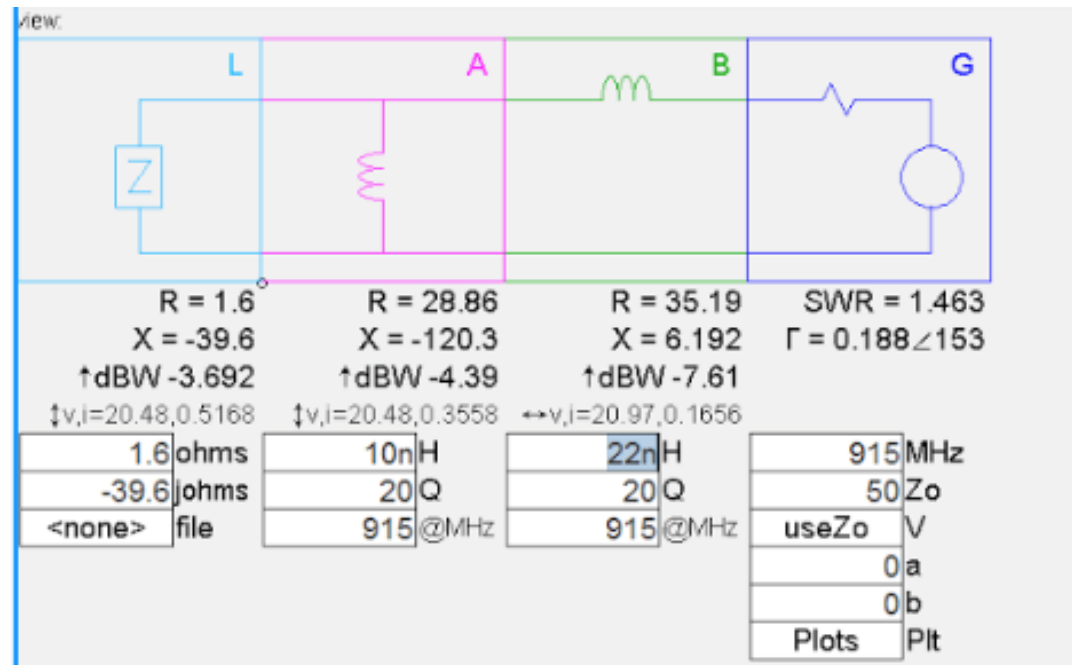
Based on 2 inductors.
Actually a better design



Step ???

Add in the shunt L, 10 nH

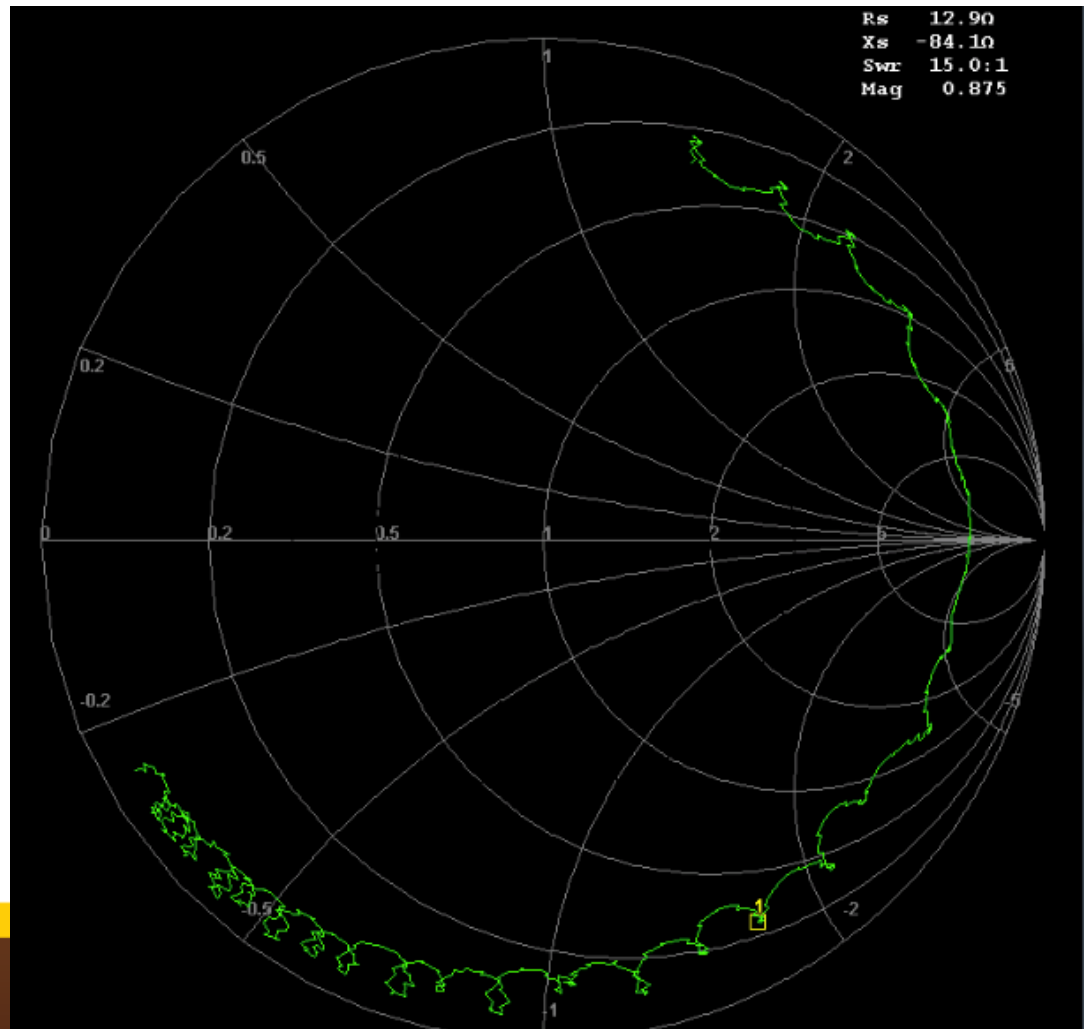
Seems a bit low. Let's reduce the inductance a hair.



Step ???


Add in the shunt L, 10 nH

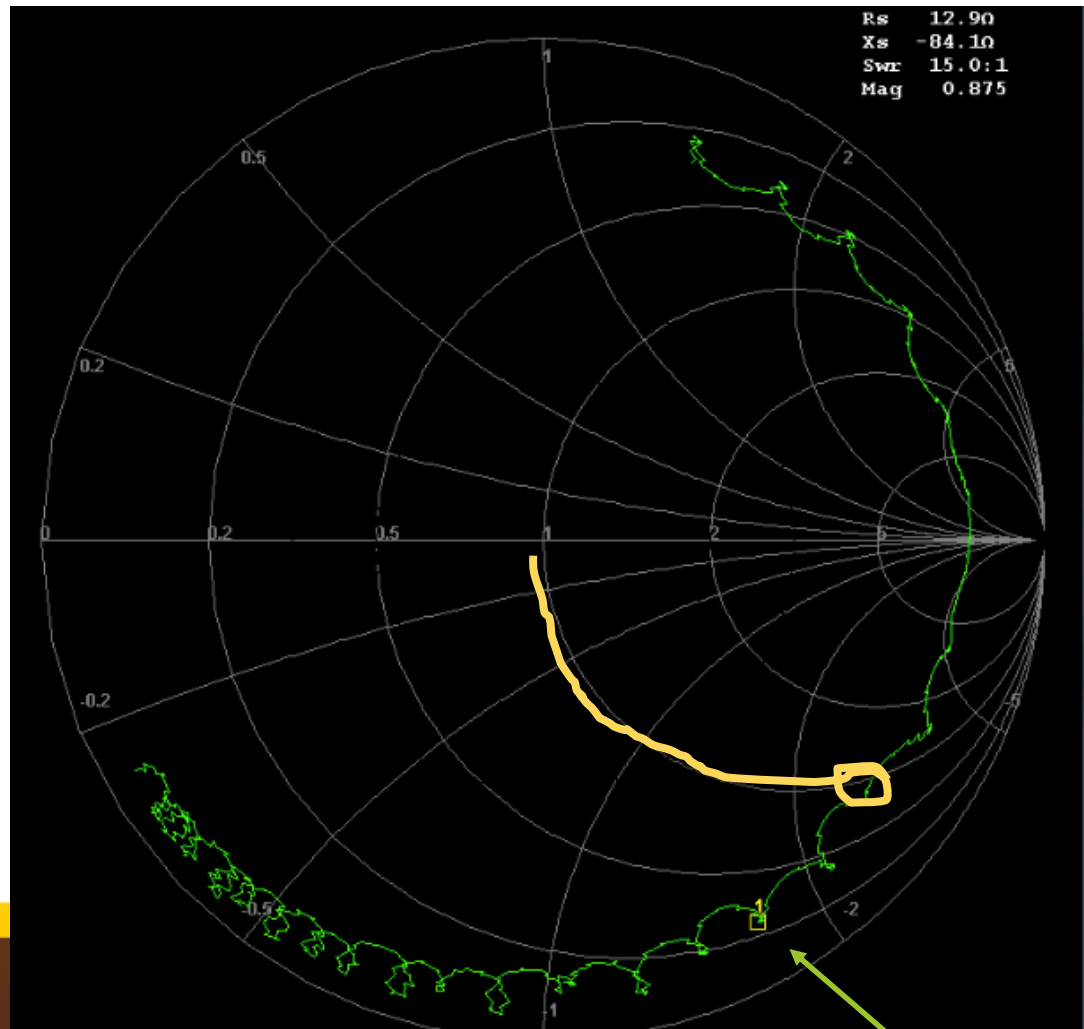Seems a bit low. Let's reduce the inductance a hair.



Step ???++

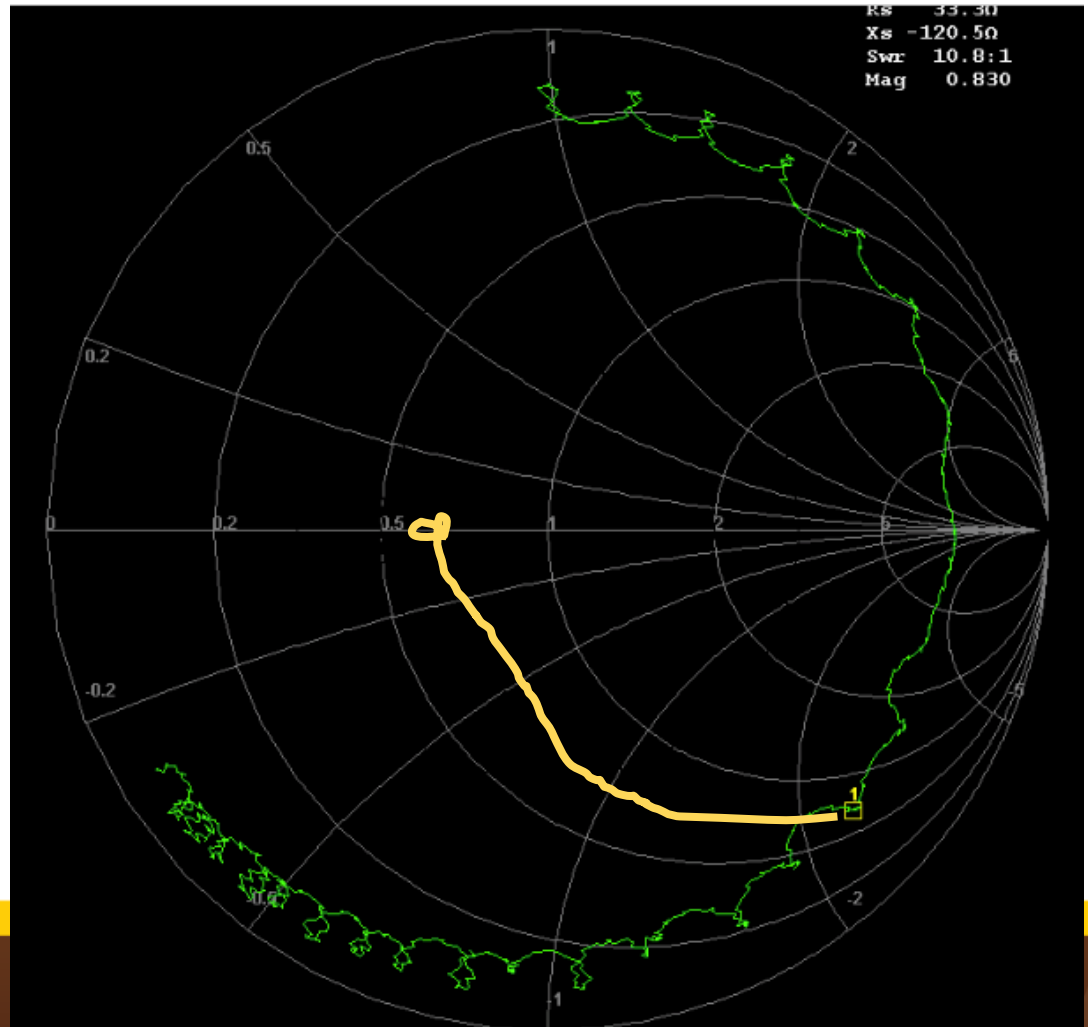Trying 8.2 nH. Looks good, but seems to add just a bit of capacitance.



Step Alpeh

Add in the next value ...


Step Alpeh

Add in the next value ...

And claim success!!

The middle of the Smith chart is good.


How good of a match is it?

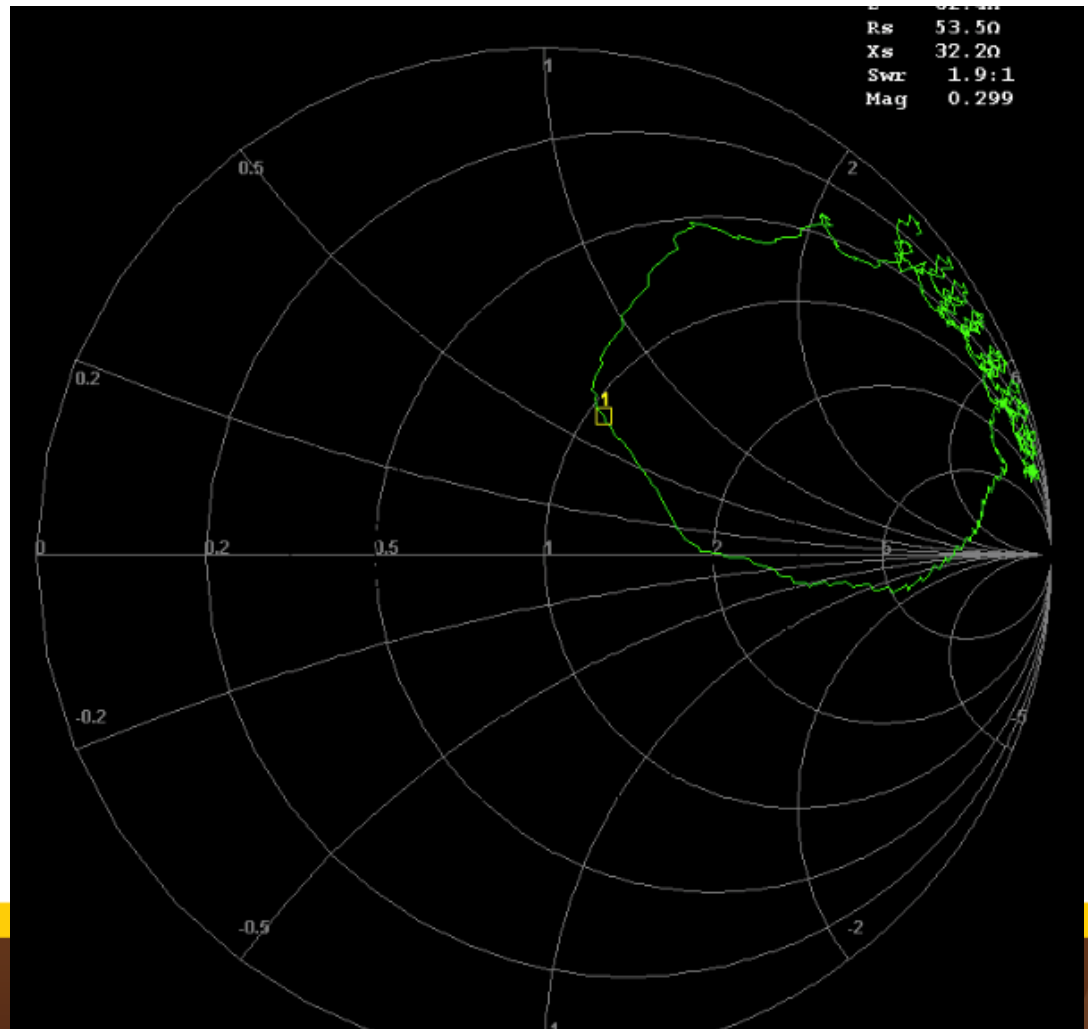

Return Loss

Magnitude of Gamma in
decibels

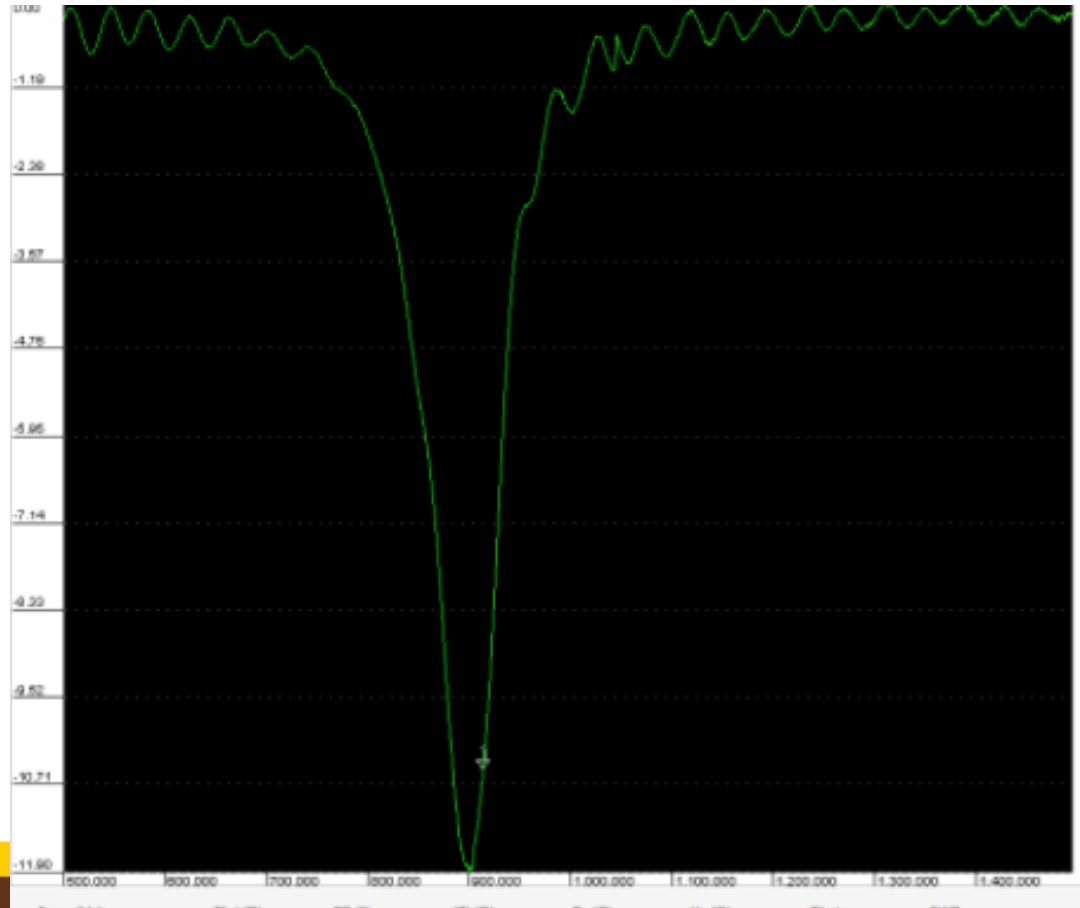Low means lower magnitude of
Gamma. Meaning less power is
being reflected and
consequently, more power is
being absorbed by the load.



Step The End

Final component values are:

- A shunt **8.2 nH near the load**. Then a series **22 nH**. Brings the circuit fairly close to 50Ω , our goal.
- Different from your values because ... diodes. We will cover this in a future lecture.