

# ECE 490-ST

## Wireless Computing

### Lesson 6 :: Impedance Transforming

# Eyeballing impedance shifts

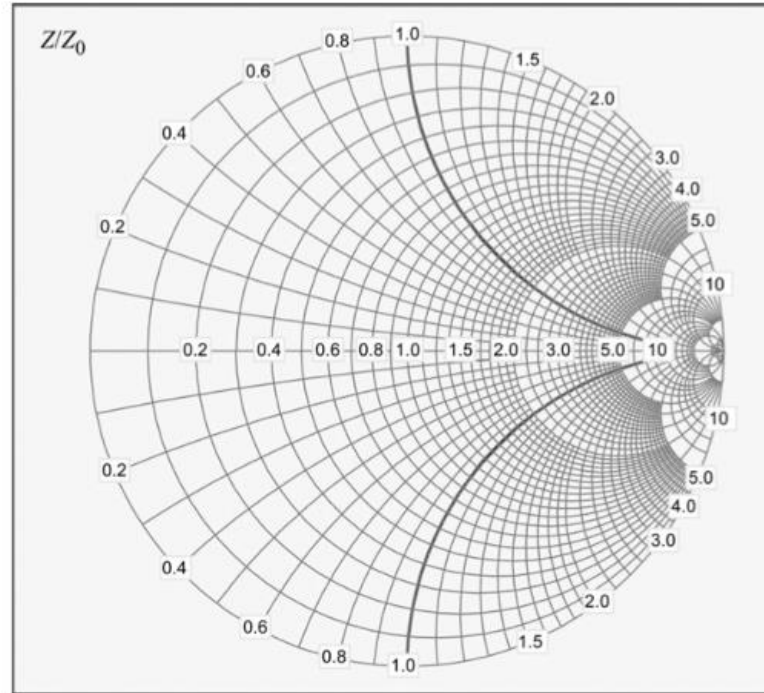


Figure A4.4



Valparaiso  
University

# Eyeballing Impedance Shifts

- If Gamma moves .25 around the Smith chart —

- $X = j \omega L$

- $X = -j / (\omega C)$

- $X = \omega L$

- $X = -1 / (\omega C)$

- $L = (X * Z_0) / \omega$

- $C = -1 / (Z_0 * X * \omega)$

$$L = \frac{0.25 * 50}{2\pi(915e6)} \\ = 1.4 \text{ nH}$$

- EX: We move from 0 -> 1.1. At 915 MHz:

- $L = (1.1 * 50) / (2 * \pi * 915e6)$


- $L = 9.566 \text{ nH}$

# VNA DEMO

What is my hand acting like?


What is the value of my hand?

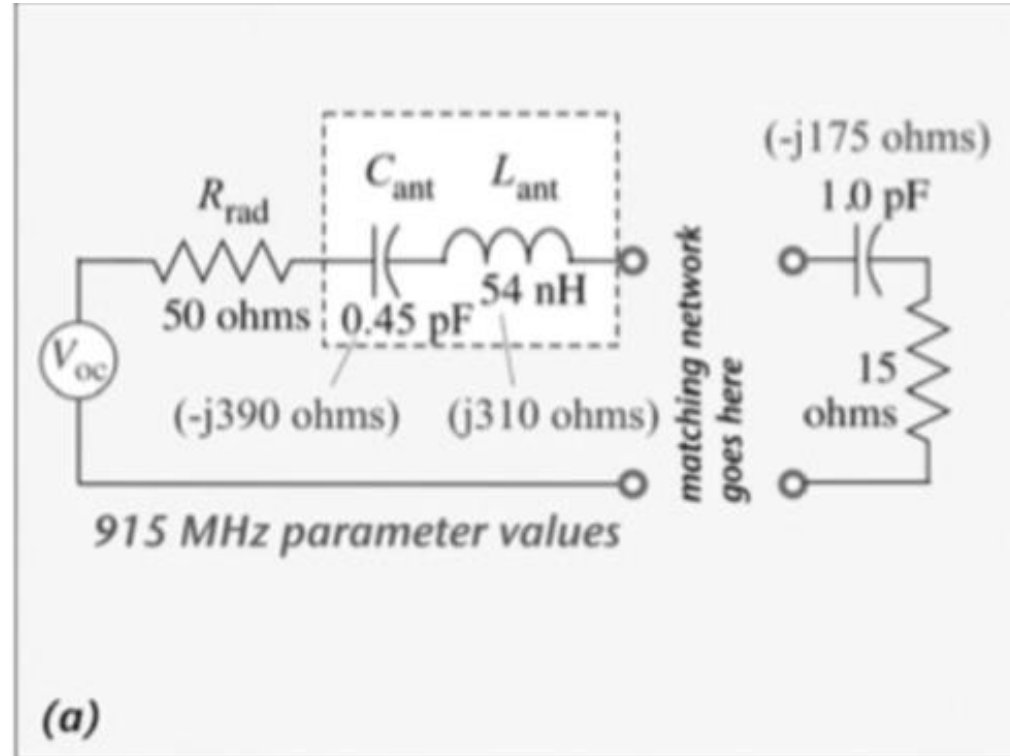I want the load to appear as the conjugate of source


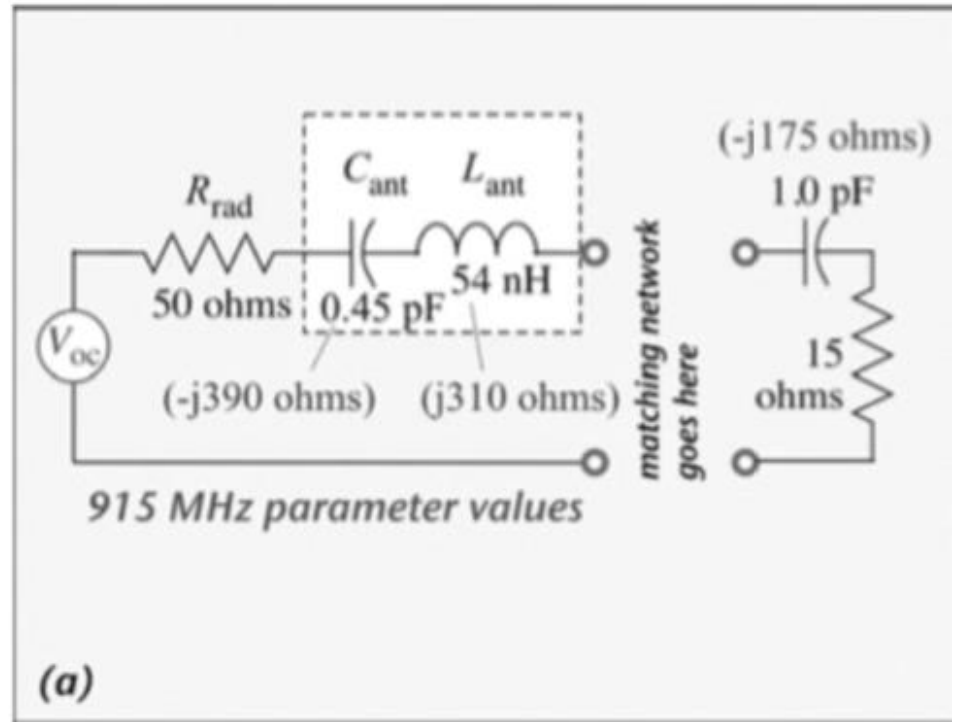
# IMPEDANCE TRANSFORMING

- What is Gamma when looking into the source?
- What is the conjugate of the input Gamma?
- What is Gamma when looking into the load?
- Which way do we need to rotate?
- Can we get there with 1 element?
- What other element do we need?



# Transforming impedances

- For impedance transformation networks, **we will only use L and C**
- These elements do not absorb energy.
- However, the job of a RESISTOR is to convert current into heat.
- We do not want that
- We don't want to lose power.
- So, **NO RESISTORS** in impedance transformation circuits



# For homework<sup>1</sup>

- Be ready to find networks (circuits) that can transform impedances.
- By inspection and small calculations
- Verify with numerical tool (MATLAB) and plotting tools (Your handy dandy Smith chart)

<sup>1</sup> At least a part of it



# Introducing Q

- ¿Qué?



# Introducing Q

- Not him either




# Introducing Q – the Quality Factor

- Q let's us quantify the bandwidth of a network


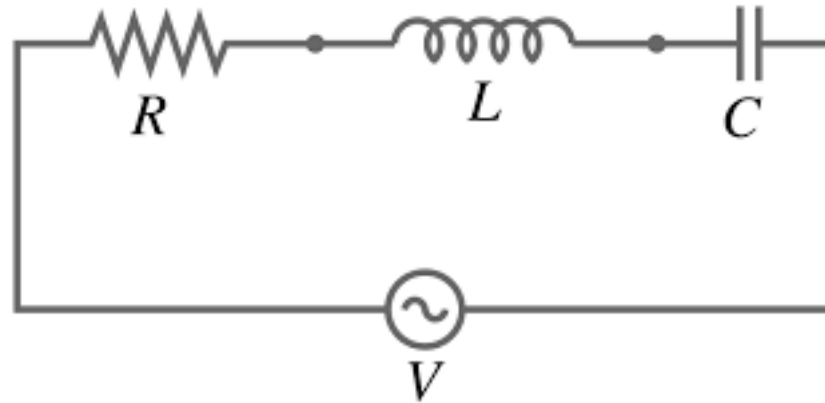
# Introducing Q – the Quality Factor

- Q let's us quantify the bandwidth of a network




- Take an RLC circuit

$$Z = R + j\omega L - \frac{j}{\omega C}$$
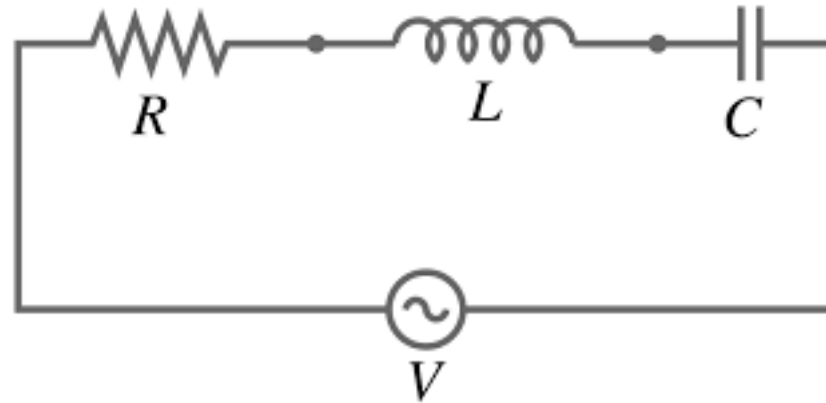
# Introducing Q – the Quality Factor

- Q let's us quantify the bandwidth of a network




$$W_{res} L = \frac{1}{W_{res} C}$$

$$W_{res} = \sqrt{\frac{1}{LC}}$$

$$Z = R + j\omega L - \frac{j}{\omega C}$$
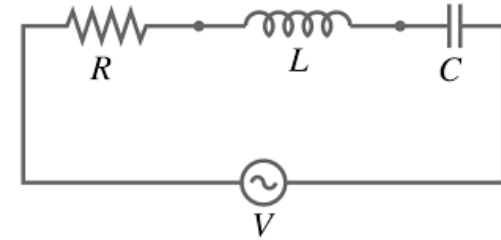
# Introducing Q – the Quality Factor

- Q let's us quantify the bandwidth of a network
- The ratio of reactance to resistance is Q.
- The lower the resistance, the less energy loss
- Q is inversely proportional to Bandwidth
- High Q means a narrower bandwidth
- For you, it just means you can calculate resistance



$$Z = R + j\omega L - \frac{j}{\omega C}$$

$$\omega_{res} L = \frac{1}{\omega_{res} C}$$

$$\omega_{res} = \sqrt{\frac{1}{LC}}$$



# Introducing Q – the Quality Factor

- For you, it just means you can calculate resistance

$$Q = \frac{\omega_{\text{res}} L}{R}$$
$$= \frac{1}{\omega_{\text{res}} C R}$$

$$\omega_{\text{res}} L = \frac{1}{\omega_{\text{res}} C}$$
$$\Rightarrow \omega_{\text{res}} = \sqrt{\frac{1}{LC}}$$

# Introducing Q – the Quality Factor

- For you, it just means you can calculate resistance

$$Q = \frac{\omega_{\text{res}} L}{R}$$
$$= \frac{1}{\omega_{\text{res}} C R}$$

- For a capacitor:  $R = \frac{1}{2\pi f C Q}$

- Find R, then add back into circuit in series with the capacitor


$$\omega_{\text{res}} L = \frac{1}{\omega_{\text{res}} C}$$
$$\Rightarrow \omega_{\text{res}} = \sqrt{\frac{1}{LC}}$$




# Designing Transformation Networks

- Most inductors or capacitors will specify a Q value.
- You do not have access to *every possible* L and C value
- Need to get as close as possible.
- Common Networks are


TEE Network

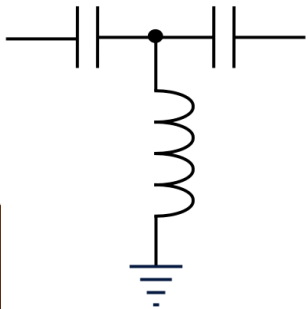

PI Network

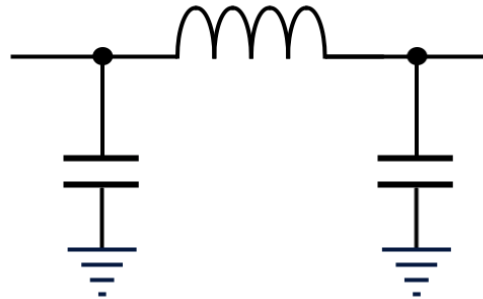

L Network

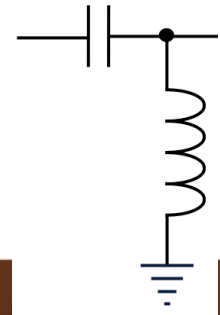

Valparaiso  
University

# Useful equations to know

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Given load  
impedance,  
Find reflection  
coefficient

$$Z_L = Z_0 \frac{1 + \Gamma}{1 - \Gamma}$$

Given reflection  
coefficient,  
Find load  
impedance

$$Q = \frac{\omega L}{R}$$
$$= \frac{1}{\omega C R}$$

Given Q &  
frequency, solve  
to find series R

# For Homework (the 2<sup>nd</sup> part)

- Design a network to transform the load impedance to 50 Ohms (at 915 MHz)
  - You are limited to L and C only, and only a small set of values
  - Find the network that you think works best and justify this (i.e., compare to other networks)
  - Once you've designed your network, implement the network and use MATLAB to apply it to the measured data to predict how it will perform.